

Example 4.9: DC Series Motor

Controlling speed of DC series motor by Resistance

Dummy unit: $\Omega \equiv 1$ $\text{rpm} \equiv 1$ $V \equiv 1$ $A \equiv 1$ $\text{Hz} \equiv 1$ $\text{kW} \equiv 10^3$ $\text{Nm} \equiv 1$ $W \equiv 1$ $k \equiv 10^3$

$$V_t := 220 \cdot V \quad R_a := 0.6\Omega \quad R_{sr} := 0.4\Omega$$

(a)

$$\text{At the point 1: } V_{t1} := 220 \cdot V \quad I_{a1} := 25 \cdot A \quad R_{ae1} := 0 \quad N_{m1} := 300\text{rpm}$$

$$E_{a1} := V_{t1} - I_{a1} \cdot (R_a + R_{sr} + R_{ae1}) \quad E_{a1} = 195 \text{ V}$$

$$P_1 := E_{a1} \cdot I_{a1} \quad P_1 = 4.875 \text{ kW}$$

$$\omega_{m1} := \frac{N_{m1}}{60} \cdot 2\pi \quad T_1 := \frac{E_{a1} \cdot I_{a1}}{\omega_{m1}} \quad T_1 = 155.176 \text{ Nm}$$

(b)

$$\text{At the point 2: } V_{t2} := V_{t1} \quad N_{m2} := 200\text{rpm}$$

Relationship between T and ω that is given by load torque characteristics.

Load torque characteristic is given as: $T = k \cdot \omega_m^2$

$$\text{It can also be stated as: } \frac{T_2}{T_1} = \left(\frac{\omega_{m2}}{\omega_{m1}}\right)^2 \quad \text{or} \quad \frac{T_2}{T_1} = \left(\frac{N_{m2}}{N_{m1}}\right)^2$$

$$T_2 := \left(\frac{N_{m2}}{N_{m1}}\right)^2 \cdot T_1 \quad T_2 = 68.967 \text{ Nm}$$

Relationship between T and I_a is given by motor torque equation.

$$T = K_{sr} \cdot I_a^2$$

$$\text{At the point 1: } T_1 = 155.176 \text{ Nm} \quad I_{a1} = 25 \text{ A}$$

$$K_{sr} := \frac{T_1}{I_{a1}^2} \quad K_{sr} = 0.248$$

Relationship between T and ω that is given by motor torque characteristics.

$$\omega_m = \frac{V_t}{\sqrt{K_{sr}} \cdot \sqrt{T}} - \frac{R_a + R_{sr} + R_{ae}}{K_{sr}}$$

At the point 2: $\omega_{m2} := \frac{N_{m2}}{60} \cdot 2\pi$ $T_2 = 68.967 \text{ Nm}$

$$R_{ae2} := \left(\frac{V_t}{\sqrt{K_{sr}} \cdot \sqrt{T_2}} - \omega_{m2} \right) \cdot K_{sr} - (R_a + R_{sr}) \quad R_{ae2} = 7 \Omega$$

$$P_2 := T_2 \cdot \omega_{m2} \quad P_2 = 1.444 \text{ kW}$$

