

## Solution For Test #2

### Question 2: Induction Machine Exact Approach

Dummy unit:  $\Omega \equiv 1$  rpm  $\equiv 1$  V  $\equiv 1$  A  $\equiv 1$  Hz  $\equiv 1$  kW  $\equiv 10^3$  Nm  $\equiv 1$  W  $\equiv 1$  k  $\equiv 10^3$

Y-connected Induction Machine:



$$V_{3\phi} := 415\text{V} \quad N_r := 1400\text{rpm} \quad f := 50\text{Hz}$$

$$R_1 := 0.25\Omega \quad R_2 := 0.20\Omega \quad p := 4$$

$$X_1 := 0.55 \quad X_2 := 0.45 \quad X_m := 50\Omega$$

$$V_1 := \frac{V_{3\phi}}{\sqrt{3}} \quad V_1 = 239.6\text{V} \quad N_s := \frac{120 \cdot f}{p} \quad N_s = 1.5 \times 10^3 \text{rpm}$$

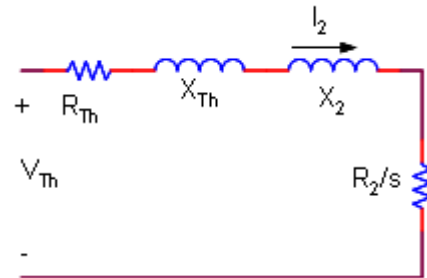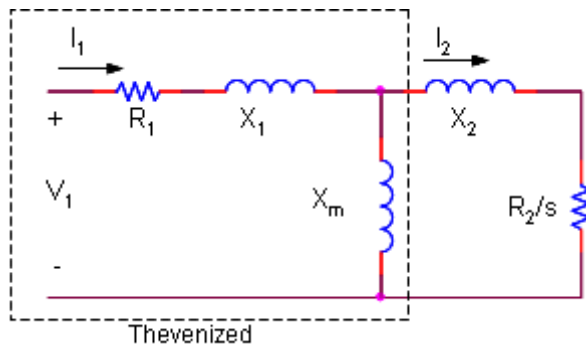We use the exact equivalent circuit first, followed by the approximate equivalent circuit for comparison.



Equivalent circuit of induction machine (based on IEEE)

Thevenin's equivalent circuit

$$V_{Th} := \frac{X_m}{\left[ R_1^2 + (X_1 + X_m)^2 \right]^{\frac{1}{2}}} \cdot V_1$$

$$V_{Th} = 236.991\text{V}$$

$$Z_{Th} := \frac{j \cdot X_m \cdot (R_1 + j \cdot X_1)}{R_1 + j \cdot (X_1 + X_m)} \quad Z_{Th} = 0.245 + 0.545i \quad |Z_{Th}| = 0.598 \quad \arg(Z_{Th}) = 1.149$$

$$R_{Th} := \text{Re}(Z_{Th}) \quad R_{Th} = 0.245\Omega \quad X_{Th} := \text{Im}(Z_{Th}) \quad X_{Th} = 0.545\Omega$$

We know that Thevenin's theorem modifies the circuit. In this case,  $I_1$  is missing in Thevenin's equivalent. Our approach (as in the textbook) is that we use Thevenin's equivalent circuit to find  $I_{2\text{prime}}$ . But, to find  $I_1$ , we will use the original circuit.

In Mathcad it is hard to write  $I_2$  prime; hence it is written without prime for the sake of convenience.

#### (a) Exact approach

(i) The line current at the point A **5 marks**

$$\text{Point A is at start} \quad s := 1 \quad R_2 \cdot \frac{(1-s)}{s} = 0$$

$$Z_{\text{total}} := R_1 + j \cdot X_1 + \frac{j \cdot X_m \cdot \left( \frac{R_2}{s} + j \cdot X_2 \right)}{\frac{R_2}{s} + j \cdot (X_2 + X_m)}$$

The impedance seen by the voltage source  $V_1$ .

$$Z_{\text{total}} = 0.446 + 0.997i \quad |Z_{\text{total}}| = 1.092 \quad \arg(Z_{\text{total}}) = 65.873 \text{ deg}$$

$$I_1 := \frac{V_1}{Z_{\text{total}}} \quad I_1 = 89.674 - 200.213i \quad |I_1| = 219.378 \quad \arg(I_1) = -65.873 \text{ deg}$$

(ii) power factor

$$\theta := \arg(I_1) \quad \theta = -65.873 \text{ deg} \quad \text{pf} := \cos(\theta) \quad \text{pf} = 0.409 \text{ lagging}$$

### (a) Approximate approach

(i) The line current at the point A

$$V_1 := \frac{V_{3\phi}}{\sqrt{3}} \quad V_1 = 239.6 \text{ V}$$

$$I_2 := \frac{V_1}{R_1 + \frac{R_2}{s} + j \cdot (X_1 + X_2)} \quad I_2 = 89.663 - 199.252i \quad |I_2| = 218.497 \text{ A} \quad \arg(I_2) = -65.772 \text{ deg}$$

$$I_m := \frac{V_1}{j \cdot X_m} \quad I_m = -4.792i \quad |I_m| = 4.792 \quad \arg(I_m) = -90 \text{ deg}$$

$$I_1 := I_m + I_2 \quad I_1 = 89.663 - 204.044i \quad |I_1| = 222.875 \quad \arg(I_1) = -66.278 \text{ deg}$$

Starting current,  $I_{\text{start}} := |I_1| \quad I_{\text{start}} = 222.875 \text{ A}$

(ii) power factor

$$\theta := \arg(I_1) \quad \theta = -66.278 \text{ deg} \quad \text{pf} := \cos(\theta) \quad \text{pf} = 0.402 \text{ lagging}$$

### (b) Exact approach

(i) Input power at the point C 5 marks

Point C is full-load. Full load slip  $s := \frac{N_s - N_r}{N_s} \quad s = 0.067$

$$Z_{\text{total}} := R_1 + j \cdot X_1 + \frac{j \cdot X_m \cdot \left( \frac{R_2}{s} + j \cdot X_2 \right)}{\frac{R_2}{s} + j \cdot (X_2 + X_m)}$$

The impedance seen by the voltage source  $V_1$ .

$$Z_{\text{total}} = \frac{R_2}{s} + j \cdot (X_2 + X_m)$$

$$Z_{\text{total}} = 3.186 + 1.171i \quad |Z_{\text{total}}| = 3.395 \quad \arg(Z_{\text{total}}) = 20.172 \text{ deg}$$

$$I_1 := \frac{V_1}{Z_{\text{total}}} \quad I_1 = 66.254 - 24.34i \quad |I_1| = 70.584 \quad \arg(I_1) = -20.172 \text{ deg}$$

$$\theta := \arg(I_1) \quad \theta = -20.172 \text{ deg} \quad \text{pf} := \cos(\theta) \quad \text{pf} = 0.939 \quad \text{lagging}$$

$$\text{Input power:} \quad P_{\text{input}} := 3 |V_1| \cdot |I_1| \cdot \text{pf} \quad P_{\text{input}} = 47.623 \text{ kW}$$

$$I_2 := \frac{V_{\text{Th}}}{R_{\text{Th}} + \frac{R_2}{s} + j \cdot (X_{\text{Th}} + X_2)} \quad I_2 = 66.761 - 20.478i \quad |I_2| = 69.831 \text{ A} \quad \arg(I_2) = -17.053 \text{ deg}$$

$$P_{\text{rot}} := 1500 \text{ W} \quad \text{rotational losses (windage plus friction)}$$

$$\text{Air gap power:} \quad P_{\text{ag}} := \frac{3 (|I_2|)^2 \cdot R_2}{s} \quad P_{\text{ag}} = 43.887 \text{ kW}$$

$$\text{Rotor Copper loss:} \quad P_2 := s \cdot P_{\text{ag}} \quad P_2 = 2.926 \times 10^3$$

$$\text{Mechanical power:} \quad P_m := (1 - s) \cdot P_{\text{ag}} \quad P_m = 40.961 \text{ kW}$$

$$\text{Output power:} \quad P_{\text{out}} := P_m - P_{\text{rot}} \quad P_{\text{out}} = 39.461 \text{ kW}$$

$$\text{Motor efficiency,} \quad \text{Eff}_{\text{motor}} := \frac{P_{\text{out}}}{P_{\text{input}}} \cdot 100 \quad \text{Eff}_{\text{motor}} = 82.861$$

## Approximate approach

(i) Input power at the point C

$$I_2 := \frac{V_1}{R_1 + \frac{R_2}{s} + j \cdot (X_1 + X_2)} \quad I_2 = 67.347 - 20.722i \quad |I_2| = 70.463 \text{ A} \quad \arg(I_2) = -17.103 \text{ deg}$$

$$I_m := \frac{V_1}{j \cdot X_m} \quad I_m = -4.792i \quad |I_m| = 4.792 \quad \arg(I_m) = -90 \text{ deg}$$

$$I_1 := I_m + I_2 \quad I_1 = 67.347 - 25.514i \quad |I_1| = 72.018 \quad \arg(I_1) = -20.749 \text{ deg}$$

$$\theta := \arg(I_1) \quad \theta = -20.749 \text{ deg} \quad \text{pf} := \cos(\theta) \quad \text{pf} = 0.935 \quad \text{lagging}$$

$$\text{Input power:} \quad P_{\text{input}} := 3 |V_1| \cdot |I_1| \cdot \text{pf} \quad P_{\text{input}} = 48.409 \text{ kW}$$

(ii) Motor Efficiency

$$P_{\text{rot}} := 1500\text{W} \quad \text{rotational losses (windage plus friction)}$$

$$\text{Air gap power:} \quad P_{\text{ag}} := \frac{3 \left( |I_2| \right)^2 \cdot R_2}{s} \quad P_{\text{ag}} = 44.685 \text{ kW}$$

$$\text{Rotor Copper loss:} \quad P_2 := s \cdot P_{\text{ag}} \quad P_2 = 2.979 \times 10^3$$

$$\text{Mechanical power:} \quad P_m := (1 - s) \cdot P_{\text{ag}} \quad P_m = 41.706 \text{ kW}$$

$$\text{Output power:} \quad P_{\text{out}} := P_m - P_{\text{rot}} \quad P_{\text{out}} = 40.206 \text{ kW}$$

$$\text{Motor efficiency,} \quad \text{Eff}_{\text{motor}} := \frac{P_{\text{out}}}{P_{\text{input}}} \cdot 100 \quad \text{Eff}_{\text{motor}} = 83.055$$

### Exact approach

(c) (i) Air gap power and developed torque at the point B **5 marks**

(Point B is at which maximum torque is developed)

$$s_{\text{Tmax}} := \frac{R_2}{\sqrt{R_1^2 + (X_1 + X_2)^2}} \quad s_{\text{Tmax}} = 0.194 \quad s := s_{\text{Tmax}}$$

$$I_2 := \frac{V_{\text{Th}}}{R_{\text{Th}} + \frac{R_2}{s} + j \cdot (X_{\text{Th}} + X_2)} \quad I_2 = 115.493 - 90.125i \quad |I_2| = 146.497 \text{ A} \quad \arg(I_2) = -37.967 \text{ deg}$$

$$\text{Air gap power,} \quad P_{\text{ag}} := \frac{3 \left( |I_2| \right)^2 \cdot R_2}{s} \quad P_{\text{ag}} = 66.365 \text{ kW}$$

$$\omega_s := \frac{N_s}{60} \cdot 2\pi \quad T := \frac{P_{\text{ag}}}{\omega_s} \quad T_{\text{max}} := T \quad T_{\text{max}} = 422.495 \text{ Nm}$$

(ii) Total losses of the motor

$$\text{Stator copper loss:} \quad P_1 := 3 \cdot \left( |I_2| \right)^2 \cdot R_1 \quad P_1 = 16.096 \text{ kW}$$

$$\text{Rotor copper loss:} \quad P_2 := 3 \cdot \left( |I_2| \right)^2 \cdot R_2 \quad P_2 = 12.877 \text{ kW}$$

$$\text{Rotational losses:} \quad P_{\text{rot}} = 1.5 \text{ kW}$$

(windage and friction)

$$P_{\text{total}} := P_1 + P_2 + P_{\text{rot}} \quad P_{\text{total}} = 30.473 \text{ kW}$$

## Approximate approach

- (i) Air gap power and developed torque at the point B **5 marks**

(Point B is at which maximum torque is developed)

$$I_2 := \frac{V_1}{R_1 + \frac{R_2}{s} + j \cdot (X_1 + X_2)} \quad I_2 = 116.223 - 90.744i \quad |I_2| = 147.453 \text{ A} \quad \arg(I_2) = -37.982 \text{ deg}$$

$$\text{Air gap power, } P_{ag} := \frac{3 \left( |I_2| \right)^2 \cdot R_2}{s} \quad P_{ag} = 67.235 \text{ kW}$$

$$\omega_s := \frac{N_s}{60} \cdot 2\pi \quad T := \frac{P_{ag}}{\omega_s} \quad T_{max} := T \quad T_{max} = 428.029 \text{ Nm}$$

- (ii) Total losses of the motor

$$\text{Stator copper loss: } P_1 := 3 \cdot \left( |I_2| \right)^2 \cdot R_1 \quad P_1 = 16.307 \text{ kW}$$

$$\text{Rotor copper loss: } P_2 := 3 \cdot \left( |I_2| \right)^2 \cdot R_2 \quad P_2 = 13.045 \text{ kW}$$

$$\text{Rotational losses: } P_{rot} = 1.5 \text{ kW}$$

(windage and friction)

$$P_{total} := P_1 + P_2 + P_{rot} \quad P_{total} = 30.852 \text{ kW}$$

- (d) Speed of the motor (rotor),  $N_r$ , at the point D is synchronous speed,  $N_s$ . At this point, slip  $s = 0$ , which means that no relative motion between rotating magnetic field of the stator and rotor conductors. As such, no emf would be induced and no current would flow in the rotor conductors. Therefore, no torque would be developed. Naturally, the rotor speed would not achieve synchronous speed; the rotor speed,  $N_r$ , is always slightly less than synchronous speed.

**1.5 marks**

- (e)  $X_m$ , in both transformer and induction machine, represents magnetizing inductance. This value reflects the amount of magnetizing current required to establish flux in the magnetic circuit. The major different between magnetic circuit in transformer and induction machine is that induction machine has air gap, while transformer does not have. Due to the air gap, higher value of current is required to establish flux in the induction machine. This corresponds to lower value of  $X_m$  in induction machine.

**1.5 marks**