


Name: .....

**TEST #2**

**SKEE4633/SEE3433**

**1 hour 20 minutes**

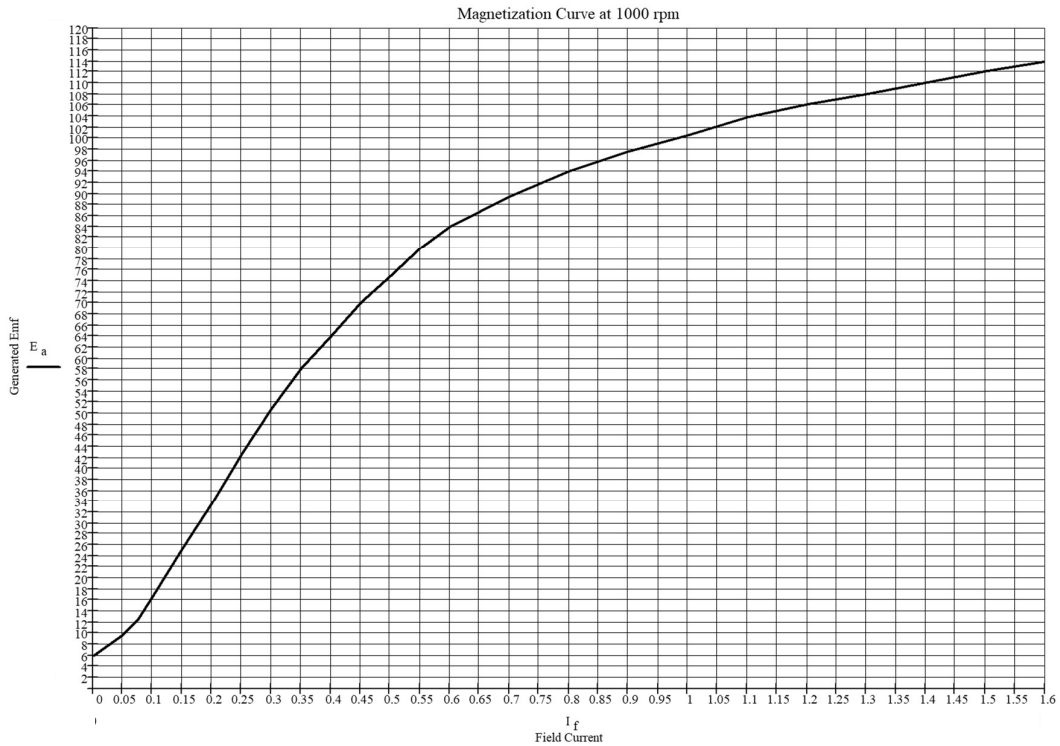Q1. The dc machine (10 kW, 100 V, 1000 rpm,  $R_a = 0.1 \Omega$ ,  $R_{fw} = 80 \Omega$ ), is connected to a 100 V dc supply and is operated as a dc shunt motor. At no-load condition, the motor runs at  $\omega_m = 1000$  rpm and  $E_a = 99$  V.



- (a) Find the speed in rpm when the rated current flows in the armature. Consider that the air gap flux is reduced by 7.5 % when rated current flows in the armature because of armature reaction. (3 marks)
- (b) Find the speed in rpm when the rated current flows in the armature. Consider that the armature reaction effect in equivalent field current,  $I_{f(AR)} = 0.10$  A. (3 marks)
- (c) What is the reduction of the flux due to the armature reaction in equivalent field current,  $I_{f(AR)}$ , for the problem in (a)? (2 marks)

Q2. A 350 V, 10 kW series motor is mechanically coupled to a fan and draws 30 A, and runs at  $\omega_1 = 600$  rpm when connected to a 350 V supply with no external resistance connected to the armature circuit (i.e.  $R_{ae1} = 0$ ). The torque required by the fan is given by  $T = k\omega^{2.25}$ , where  $k$  is a constant of proportionality.  $R_a = 0.5 \Omega$  and  $R_{sf} = 0.3 \Omega$ . Neglect armature reaction and the rotational losses.

- (a) Determine the back emf,  $E_{a1}$ , the power delivered to the fan,  $P_1$ , and the torque developed by the motor,  $T_1$ . (3 marks)
- (b) The speed is to be reduced to  $\omega_2 = 500$  rpm by inserting a resistance,  $R_{ae2}$  in the armature circuit. Determine the value of this resistance and the torque developed by the motor,  $T_2$ . (3 marks)

- (c) Sketch speed-torque characteristics ( $\omega$  versus  $T$ ) of the series DC motor for two different values of  $R_{ae}$  together with the given load profile,  $T = k\omega^{2.25}$ . Label clearly  $R_{ae1}$ ,  $R_{ae2}$ ,  $\omega_1$ ,  $\omega_2$ ,  $T_1$ , and  $T_2$  on the sketch. (2 marks)

- Q3. A 3-phase,  $\Delta$ -connected, 380 V, 47.5 kW, 50 Hz, 575 rpm, 10-pole induction motor is operating at rated conditions has an efficiency of 92 percent. The rotational loss is 1 kW and it draws a line current of 96 A. Assume that the core losses are embedded in rotational losses. Find

- Mechanical power (1 mark)
- Air gap power (1 mark)
- Rotor copper loss (1 mark)
- Input power (1 mark)
- Stator copper loss (1 mark)
- Total losses (1 marks)
- Power factor (1 mark)

- Q4. A 3-phase, 415 V (line to line), 50 Hz, 1430 rpm, 6-pole,  $\Delta$ -connected, induction motor has the following equivalent circuit constants in ohms per phase.

$$R_1 = 1.4 \Omega, R_2' = 0.6 \Omega, X_1 = 2 \Omega, X_2' = 1 \Omega \text{ and } X_m = 50 \Omega.$$

The rotational losses of the motor may be assumed to be constant at 275W, independent of load.

- Calculate the starting current and the corresponding power factor. (3 marks)
- Calculate the maximum torque. (3 marks)
- Calculate the efficiency for the full-load slip. (3 marks)

**Use the approximate equivalent circuit.**

Potentially useful formula

$$\begin{array}{lll} E_a = K_a \phi \omega & E_a = V_t - I_a R_a & \frac{E_{aFL}}{E_{aNL}} = \frac{K_a \phi \omega_{FL}}{K_a \phi \omega_{NL}} \\ P = E_a I_a & E_a = V_t - I_a (R_a + R_{sr} + R_{ae}) & E_a = K_{sr} I_a \omega_m \\ P = T \omega & T = K_{sr} I_a^2 & s = \frac{N_s - N_r}{N_s} \\ I_{f(\text{eff})} = I_f - I_{f(\text{AR})} & N_s = \frac{120f}{p} & P_{ag} = I_2'^2 \frac{R_2'}{s} \\ P_{rotor} = s P_{ag} & P_m = (1 - s) P_{ag} & \\ P_{ag} = T \omega_s & S_{Tmax} = \frac{R_2'}{\sqrt{[(R_1^2 + (X_1 + X_2)^2]}} & I_2' = \frac{V_1}{R_1 + \frac{R_2'}{s} + j(X_1 + X_2')} \end{array}$$