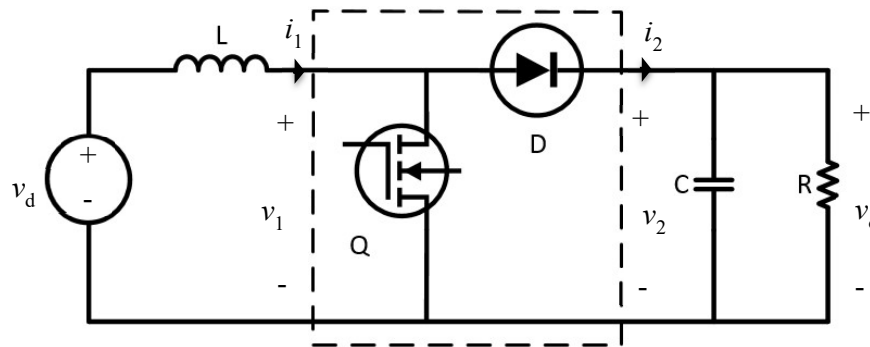


**Question 1**

- (a) What do you understand by averaged switch modeling? Explain briefly the procedure to obtain the averaged switch model. [5 marks]
- (b) In the boost converter as shown in **Figure Q1**, the averaged model of the switch network is desired. The terminals voltage and current of the switch network are given as  $v_1$ ,  $v_2$ ,  $i_1$  and  $i_2$ , respectively. The input voltage is constant,  $v_d$ . The capacitor,  $C$ , is sufficiently large so that the output voltage,  $v_o$ , can considerably be constant. The converter operates in continuous conduction mode (CCM) with inductor current repeatedly changes between  $i_{Lmin}$  and  $i_{Lmax}$  under the steady-state condition.



**Figure Q1**


- (i) Sketch the terminal switch network waveforms:  $v_1$ ,  $v_2$ ,  $i_1$  and  $i_2$ . Label all the key quantities. [5 marks]
- (ii) Find the average voltage conversion ratio,  $\langle v_2 \rangle / \langle v_1 \rangle$  and the average current conversion ratio,  $\langle i_2 \rangle / \langle i_1 \rangle$ , of the switch network. [5 marks]
- (iii) Construct averaged circuit model of the complete boost converter by replacing the switch network with the averaged switch model (DC transformer model) based on the equations found in (ii). [5 marks]
- (iv) Obtain the voltage conversion ratio,  $M_v$ , and the efficiency,  $\eta$ , of the converter in steady-state under ideal condition. [5 marks]

**Question 2**

- (a) State two types of losses occur in non-isolated DC-DC converters. Explain briefly. [5 marks]
- (b) In a buck converter, the MOSFET has the on resistance,  $R_Q$ , the diode forward voltage drop can be modeled by constant voltage  $V_D$  with resistor  $R_D$ , and the inductor has an internal resistance  $r_L$ .
- (i) Sketch an equivalent circuit, which models the DC properties of this converter. The averaged switch model can be represented by dependent sources or a DC transformer. [5 marks]
- (ii) Derive an expression for the efficiency of the converter. [6 marks]
- (iii) Derive an expression for the conversion ratio,  $M_V(D) = V_o/V_d$ . [4 marks]
- (iv) The converter is used to step-down the input voltage of  $V_d = 18$  V to the output voltage,  $V_o = 12$  V. If  $R_Q = 50$  m $\Omega$ ,  $V_D = 0.7$  V,  $R_D = 60$  m $\Omega$  and  $r_L = 0.1$   $\Omega$ , determine the efficiency of the buck converter. Also, determine the required duty ratio,  $D$ . [5 marks]

**Question 3**

- (a) What do you understand by AC small-signal model? Why do we need AC small signal model? [5 marks]
- (b) The averaged circuit model of an ideal boost converter is shown in **Figure Q3**. The boost converter has the inductor,  $L = 75 \mu\text{H}$ , capacitor,  $C = 330 \mu\text{F}$ , the input voltage,  $v_d = 12 \text{ V}$ , the output voltage,  $v_o = 18 \text{ V}$ , the load resistance,  $R = 6 \Omega$ , and the switching frequency,  $f_s = 100 \text{ kHz}$ . The circuit operates in continuous conduction mode.

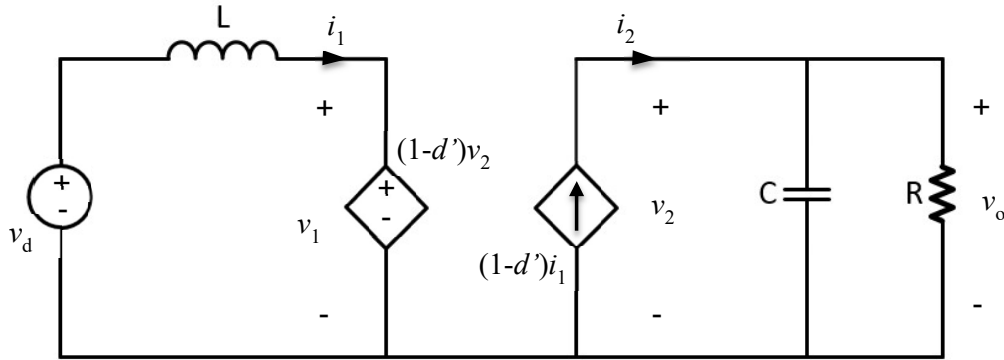

**Figure Q3**

- (i) By doing perturbation and linearization on the averaged circuit model, obtain AC small-signal model and DC steady-state model. [9 marks]
- (ii) Analyze the DC steady-state model to determine all bias point constants. [5 marks]
- (iii) Analyze the AC small signal model to obtain the control to output transfer function,  $\frac{\hat{v}_o}{\hat{d}}(s)$ . [6 marks]

**Question 4**

- (a) With the help of a functional block diagram explain the benefits of negative feedback. [5 marks]
- (b) A buck-boost converter has the inductor,  $L = 15 \mu\text{H}$ , the capacitor,  $C = 440 \mu\text{F}$ , the equivalent series resistance of capacitor,  $R_{\text{ESR}} = 20 \text{ m}\Omega$ , the input voltage,  $V_d = 12 \text{ V}$ , the output voltage,  $|v_o| = 5 \text{ V}$ , the load resistance,  $R = 2 \Omega$ , and the switching frequency,  $f_s = 200 \text{ kHz}$ . The PWM has the sawtooth peak,  $V_m = 3 \text{ V}$  and the error amplifier has the voltage reference,  $V_{\text{ref}} = 2.5 \text{ V}$ . The circuit operates in continuous conduction mode and the control to output transfer function for voltage mode control is given in **Appendix B**.

It is desired to design a voltage mode controller for the feedback system to regulate the output voltage. The controller is type-3 error amplifier, as shown in the **Appendix E**, and the calculation is based on k-factor approach. The required phase margin is at least  $45^\circ$  and the crossover frequency is at 1 kHz.

- (i) Determine the magnitude in dB and phase in degrees of the loop gain at the crossover frequency, excluding error amplifier. [9 marks]
- (ii) What are the gain and the phase boost of the error amplifier required at the crossover frequency? [5 marks]
- (iii) Determine all resistance and capacitance values of the type-3 error amplifier (see **Appendix E**). [6 marks]

**Question 5**

- (a) Explain the advantages of current mode control over voltage mode control. [5 marks]
- (b) A buck converter has the  $L = 25 \mu\text{H}$ ,  $C = 660 \mu\text{F}$ , the equivalent series resistance of capacitor,  $R_{\text{ESR}} = 20 \text{ m}\Omega$ , the input voltage,  $V_d = 12 \text{ V}$ , the output voltage,  $v_o = 5 \text{ V}$ , the load resistance,  $R = 1.25 \Omega$ , and the switching frequency  $f_s = 200 \text{ kHz}$ . The error amplifier has  $V_{\text{ref}} = 2.5 \text{ V}$ . The circuit operates in continuous conduction mode and the control to output transfer function is given in **Appendix C**.

It is desired to design a current mode controller for the outer loop of the feedback system. The controller is type-2 error amplifier, as shown in the **Appendix D**, and the calculation is based on k-factor approach. The required phase margin is at least  $65^\circ$  and the crossover frequency is at 6 kHz.

- (i) Determine the required amplitude of the external ramp. [4 marks]
- (ii) Determine the magnitude in dB and the phase in degrees of the loop gain at the crossover frequency. [8 marks]
- (iii) What are the gain and the phase boost of the error amplifier required at the crossover frequency? [3 marks]
- (iv) Determine all resistance and capacitance values of the type-2 error amplifier (see **Appendix D**). [5 marks]

Appendix A

Potentially Useful Formula

Transfer Function	With $s = j\omega$	Gain	Phase
$1 + \frac{s}{\omega_z}$	$1 + j\frac{\omega}{\omega_z}$	$\sqrt{1 + \left(\frac{\omega}{\omega_z}\right)^2}$	$\tan^{-1}\left(\frac{\omega}{\omega_z}\right)$
$1 - \frac{s}{\omega_z}$	$1 - j\frac{\omega}{\omega_z}$	$\sqrt{1 + \left(\frac{\omega}{\omega_z}\right)^2}$	$-\tan^{-1}\left(\frac{\omega}{\omega_z}\right)$
$\frac{1}{1 + \frac{s}{\omega_p}}$	$\frac{1}{1 + j\frac{\omega}{\omega_p}}$	$\frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_p}\right)^2}}$	$-\tan^{-1}\left(\frac{\omega}{\omega_p}\right)$
$\frac{1}{1 + \frac{s}{Q\omega_o} + \left(\frac{\omega}{\omega_o}\right)^2}$	$\frac{1}{1 - \left(\frac{\omega}{\omega_o}\right)^2 + j\frac{\omega}{Q\omega_o}}$	$\frac{1}{\sqrt{\left[1 - \left(\frac{\omega}{\omega_o}\right)^2\right]^2 + \left(\frac{\omega}{Q\omega_o}\right)^2}}$	$-\tan^{-1}\left(\frac{\omega/Q\omega_o}{1 - \left(\frac{\omega}{\omega_o}\right)^2}\right)$

**Appendix B**

Control to output transfer functions for voltage mode control

Converter	Control-to-output transfer function, $\frac{\hat{v}_o}{\hat{d}}$	Parameters definition
Buck	$g_{do} \frac{\left(1 + \frac{s}{\omega_{zESR}}\right)}{1 + \frac{s}{Q\omega_o} + \frac{s^2}{\omega_o^2}}$	$g_{do} = V_d ; \omega_o = \frac{1}{\sqrt{LC}}$ $\omega_{zESR} = \frac{1}{rC} ; Q = \frac{R}{\omega_o L}$
Boost	$g_{do} \frac{\left(1 - \frac{s}{\omega_{zRHP}}\right)\left(1 + \frac{s}{\omega_{zESR}}\right)}{1 + \frac{s}{Q\omega_o} + \frac{s^2}{\omega_o^2}}$	$g_{do} = \frac{V_d}{(1-D)^2} ; \omega_o = \frac{1}{\sqrt{L_{eq}C}}$ $\omega_{zESR} = \frac{1}{rC} ; \omega_{zRHP} = \frac{R}{L_{eq}}$ $Q = \frac{R}{\omega_o L_{eq}} ; L_{eq} = \frac{L}{(1-D)^2}$
Buck-boost	$g_{do} \frac{\left(1 - \frac{s}{\omega_{zRHP}}\right)\left(1 + \frac{s}{\omega_{zESR}}\right)}{1 + \frac{s}{Q\omega_o} + \frac{s^2}{\omega_o^2}}$	$g_{do} = \frac{V_d}{(1-D)^2} ; \omega_o = \frac{1}{\sqrt{L_{eq}C}}$ $\omega_{zESR} = \frac{1}{rC} ; \omega_{zRHP} = \frac{R}{DL_{eq}}$ $Q = \frac{R}{\omega_o L_{eq}} ; L_{eq} = \frac{L}{(1-D)^2}$

**Appendix C**

Control to output transfer functions,  $\frac{\hat{v}_o}{\hat{i}_L}$ , for current mode control


Converter Transfer Functions for Average Current Mode Controller

Converter	$\frac{\hat{i}_L}{\hat{d}}$	$\frac{\hat{v}_o}{\hat{i}_L}$
Buck	$\frac{V_g}{R} \frac{(1 + sRC)}{1 + s\left(\frac{L}{R} + rC\right) + s^2LC}$	$\frac{R(1 + srC)}{1 + sRC}$
Boost	$\frac{V_g}{R(1-D)^3} \frac{(2 + sRC)}{1 + s\frac{L}{R(1-D)^2} + s^2\frac{LC}{(1-D)^2}}$	$\frac{R(1-D)\left(1 - \frac{sL}{R(1-D)^2}\right)(1 + srC)}{2 + sRC}$
Buck-boost	$\frac{V_g(1+D)}{R(1-D)^3} \frac{\left(1 + \frac{1}{1+D}sRC\right)}{1 + s\frac{L}{R(1-D)^2} + s^2\frac{LC}{(1-D)^2}}$	$\frac{R(1-D)\left(1 - \frac{sLD}{R(1-D)^2}\right)(1 + srC)}{(1+D)\left(1 + \frac{1}{1+D}sRC\right)}$



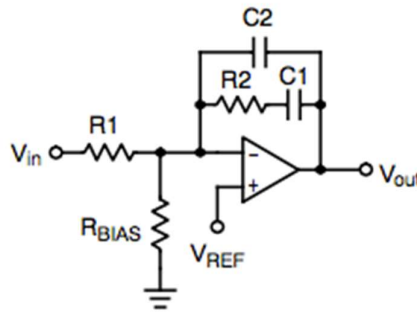**Appendix D**

K-factor approach for type 2 error amplifier



1. Calculate the gain,  $A_{co}$ , and the phase,  $P_{co}$ , of the power stage including PWM at the cross over frequency,  $f_{co}$ .
2. Calculate the phase boost,  $P_{boost}$ , required:

$$P_{boost} = PM - 90^\circ - P_{co}$$

3. Calculate k factor:

$$K = \tan\left(\frac{P_{boost}}{2} + 45^\circ\right)$$

$$G = 10^{\frac{-A_{co}}{20}}$$

4. Calculate capacitances and resistances consecutively:

$$R1 = 4.7\text{k}\Omega$$

$$R_{bias} = \frac{V_{ref} R_1}{V_o - V_{ref}}$$


$$C2 = \frac{1}{2\pi f_{co} G K R1}$$

$$C1 = C2(K^2 - 1)$$

$$R2 = \frac{K}{2\pi f_{co} C1}$$
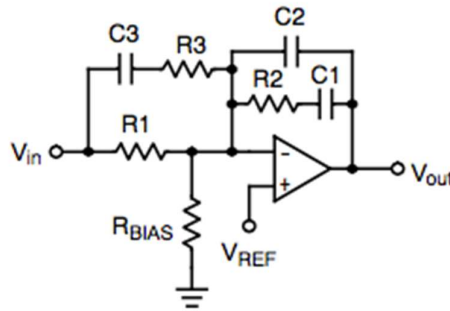
### Appendix E

K-factor approach for type 3 error amplifier



1. Calculate the gain,  $A_{co}$  (in dB), and the phase,  $P_{co}$  (in degree), of the power stage including PWM at the cross over frequency,  $f_{co}$ .
2. Calculate the amplifier phase boost,  $P_{boost}$ , and gain,  $G$ , required:

$$P_{boost} = PM - 90^\circ - P_{co}$$

$$G = 10^{\frac{-A_{co}}{20}}$$

3. Calculate K factor:

$$K = \tan^2 \left( \frac{P_{boost}}{4} + 45^\circ \right)$$

4. Calculate capacitances and resistances consecutively:

$$R1 = 4.7 \text{ k}\Omega$$

$$R_{bias} = \frac{V_{ref} R1}{V_o - V_{ref}}$$

$$C2 = \frac{1}{2\pi f_{co} G R1}$$

$$C1 = C2(K - 1)$$

$$R2 = \frac{\sqrt{K}}{2\pi f_{co} C1}$$

$$R3 = \frac{R1}{(K - 1)}$$

$$C3 = \frac{1}{2\pi f_{co} \sqrt{K} R3}$$