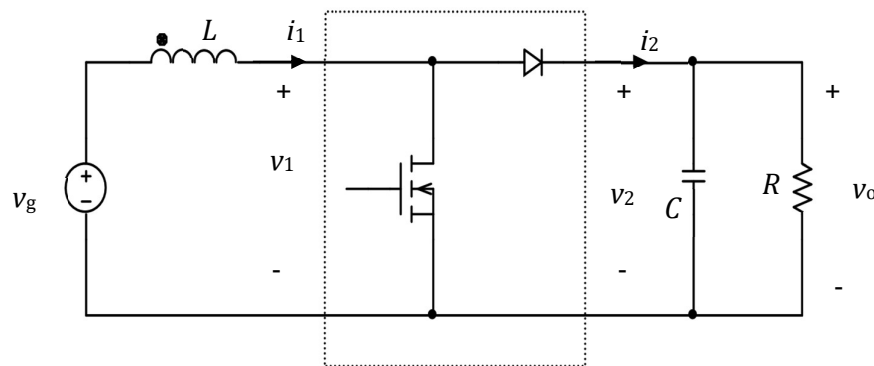


**Question 1**

In the boost converter of Figure Q1, the averaged model of the switch network is desired. The terminals voltage and current of the switch network are given as  $v_1$ ,  $v_2$ ,  $i_1$  and  $i_2$ . The input voltage is a constant,  $v_g$ . The capacitor,  $C$ , is sufficiently large so that the output voltage,  $v_o$ , is considerably constant. The converter operates in CCM with inductor current repeatedly changes between  $i_{Lmin}$  and  $i_{Lmax}$  in steady state.

**Figure Q1**

- Draw the terminal switch network waveforms:  $v_1$ ,  $v_2$ ,  $i_1$  and  $i_2$ . Label key quantities. [3 marks]
- Find the average voltage conversion ratio,  $\langle v_2 \rangle / \langle v_1 \rangle$  and the average current conversion ratio,  $\langle i_2 \rangle / \langle i_1 \rangle$  of the switch network. [2 marks]
- Construct averaged circuit model of the complete buck converter by replacement of the switch network by the averaged switch model (dependent sources) based on the equations found in (ii). [2 marks]
- If  $v_g = 10$  V,  $v_o = 15$  V and  $R = 5$   $\Omega$ , find  $\langle i_1 \rangle$ ,  $\langle i_2 \rangle$ ,  $\langle v_1 \rangle$ , and  $\langle v_2 \rangle$  under steady-state condition. [3 marks]

**Question 2**

In a buck-boost converter, the MOSFET has on resistance,  $R_Q = 65$  m $\Omega$ , the diode forward voltage drop can be modeled by constant voltage  $V_D = 0.8$  V, with resistor  $R_D = 75$  m $\Omega$ , and the inductor has an internal resistance  $r_L = 200$  m $\Omega$ . The load equivalent resistance  $R = 10$   $\Omega$ . The input voltage,  $v_g = 40$  V and the output voltage,  $|v_o| = 30$  V.

- Draw an equivalent circuit which shows the DC properties of this converter. The averaged switch model can be represented by dependent sources or a DC transformer. [2 mark]
- Derive the efficiency,  $\eta$ , and the voltage conversion ratio,  $M_v$ . [3 marks]

(iii) Use SECANT method to determine the required duty cycle,  $D$ . [3 marks]

(iv) Determine the efficiency of the converter. [2 marks]

### Question 3

Show that the efficiency,  $\eta$ , for the buck converter including the inductor resistance,  $R_L$ , and the diode forward voltage drop,  $V_D$ , is given by

$$\eta = \frac{1}{1 + \frac{R_L}{R} + \frac{(1-D)V_D}{V_o}}$$

Based on the equation, Suggest ONE method to improve the efficiency of the buck converter for the low voltage application.

[4 marks]

---

#### Potentially Use Formula

$$D_{k+1} = D_k - f(D_k) \frac{D_k - D_{k-1}}{f(D_k) - f(D_{k-1})} \quad D_0 = D_{ideal} \quad D_1 = D_{ideal} + 0.1$$

$$\eta = \frac{1}{1 + \frac{P_{loss}}{P_o}} = M_V M_I$$

$$R_{EQ} = r_L + DR_Q + D'R_D$$

$$V_{EQ} = DV_Q + D'V_D$$

$$\int_0^T v_L dt = 0$$

$$\frac{1}{L} \int_0^{DT} v_L dt = \Delta i_L$$

$$-\frac{1}{L} \int_{DT}^T v_L dt = \Delta i_L$$

$$\frac{V_o}{V_g} = D, \frac{V_o}{V_g} = \frac{1}{1-D}, \frac{V_o}{V_g} = \frac{D}{1-D}$$