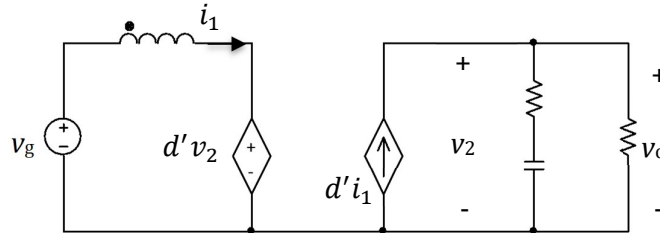


Question 1

The averaged circuit model of an ideal boost converter is shown in Figure Q1. The boost converter has $L = 25 \mu\text{H}$, $C = 660 \mu\text{F}$, $r_{\text{ESR}} = 50 \text{ m}\Omega$, input voltage, $v_g = 20 \text{ V}$, output voltage, $v_o = 30 \text{ V}$, load resistance, $R = 15 \Omega$, and switching frequency $f_s = 100 \text{ kHz}$. The circuit operates in continuous conduction mode.

**Figure Q1**

- (i) By doing perturbation and linearization on the averaged circuit model, obtain AC small-signal and DC steady-state model models. [6 marks]
- (ii) Analyze DC steady-state model to determine all bias point constants. [3 marks]
- (iii) Based on the transfer function for the boost converter in **Table II**, find g_{d_o} , f_o , Q , $f_{z\text{ESR}}$, and $f_{z\text{RHP}}$. Sketch Bode plot for the gain and phase and label key quantities. [5 marks]

Question 2

The boost converter in Question 1 is required to design a controller to regulate the output voltage. The PWM has the sawtooth peak $V_m = 4 \text{ V}$ and the error amplifier has $V_{\text{ref}} = 3 \text{ V}$.

It is desired to design a type-3 error amplifier based on pole-zero placement procedure as in **Appendix A**, that will give the crossover frequency, $f_{co} = 4 \text{ kHz}$ and the phase margin, $\text{PM} = 50^\circ$. The poles and zeros of the error amplifier are placed as follows: (i) the two zeros (f_{z1} and f_{z2}) are placed at f_o , (ii) the first pole, f_{p1} is placed at $f_{z\text{RHP}}$, (iii) The second pole, f_{p2} , is placed as in the Appendix A.

- (i) Determine the magnitude in dB, A_{codb} , and phase in degrees, P_{co} , of the boost converter (including PWM) at the crossover frequency. [[7 marks]
- (ii) Determine the phase boost, P_{boost} , required, the location of the second pole of error amplifier, f_{p2} and the gain of the integrator, ω_i . [5 marks]
- (iii) Determine all resistance and capacitance values of the type-3 error amplifier (see Appendix A). [4 marks]

Potentially Useful Formula

Table I

Transfer Function	With $s = j\omega$	Gain	Phase
$1 + \frac{s}{\omega_z}$	$1 + j\frac{\omega}{\omega_z}$	$\sqrt{1 + \left(\frac{\omega}{\omega_z}\right)^2}$	$\tan^{-1}\left(\frac{\omega}{\omega_z}\right)$
$1 - \frac{s}{\omega_z}$	$1 - j\frac{\omega}{\omega_z}$	$\sqrt{1 + \left(\frac{\omega}{\omega_z}\right)^2}$	$-\tan^{-1}\left(\frac{\omega}{\omega_z}\right)$
$\frac{1}{1 + \frac{s}{\omega_p}}$	$\frac{1}{1 + j\frac{\omega}{\omega_p}}$	$\frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_p}\right)^2}}$	$-\tan^{-1}\left(\frac{\omega}{\omega_p}\right)$
$\frac{1}{1 + \frac{s}{Q\omega_o} + \frac{s^2}{\omega_o^2}}$	$\frac{1}{1 - \left(\frac{\omega}{\omega_o}\right)^2 + j\frac{\omega}{Q\omega_o}}$	$\frac{1}{\sqrt{\left[1 - \left(\frac{\omega}{\omega_o}\right)^2\right]^2 + \left(\frac{\omega}{Q\omega_o}\right)^2}}$	$-\tan^{-1}\left(\frac{\frac{\omega/Q\omega_o}{1 - \left(\frac{\omega}{\omega_o}\right)^2}\right)$

Table 2

Converter	Control-to-output transfer function, $\frac{\hat{v}_o}{\hat{d}}$	Parameters definition
Buck	$g_{do} \frac{\left(1 + \frac{s}{\omega_{zESR}}\right)}{1 + \frac{s}{Q\omega_o} + \frac{s^2}{\omega_o^2}}$	$g_{do} = V_d$; $\omega_o = \frac{1}{\sqrt{LC}}$ $\omega_{zESR} = \frac{1}{r_{ESR}C}$; $Q = R\sqrt{\frac{C}{L}}$
Boost	$g_{do} \frac{\left(1 - \frac{s}{\omega_{zRHP}}\right)\left(1 + \frac{s}{\omega_{zESR}}\right)}{1 + \frac{s}{Q\omega_o} + \frac{s^2}{\omega_o^2}}$	$g_{do} = \frac{V_d}{(1-D)^2}$; $\omega_o = \frac{1}{\sqrt{L_{eq}C}}$ $\omega_{zESR} = \frac{1}{r_{ESR}C}$; $\omega_{zRHP} = \frac{R}{L_{eq}}$ $Q = R\sqrt{\frac{C}{L_{eq}}}$; $L_{eq} = \frac{L}{(1-D)^2}$
Buck-boost	$g_{do} \frac{\left(1 - \frac{s}{\omega_{zRHP}}\right)\left(1 + \frac{s}{\omega_{zESR}}\right)}{1 + \frac{s}{Q\omega_o} + \frac{s^2}{\omega_o^2}}$	$g_{do} = \frac{V_d}{(1-D)^2}$; $\omega_o = \frac{1}{\sqrt{L_{eq}C}}$ $\omega_{zESR} = \frac{1}{r_{ESR}C}$; $\omega_{zRHP} = \frac{R}{DL_{eq}}$ $Q = R\sqrt{\frac{C}{L_{eq}}}$; $L_{eq} = \frac{L}{(1-D)^2}$

Appendix A

Design of the type III compensator using pole-zero placement: Boost

Given desired crossover frequency, f_{co} , and phase margin, PM, and the power stage gain, A_{co} , and phase, P_{co} , at the crossover frequency:

(i) The phase boost required by the compensator at the crossover frequency is

$$P_{boost} = PM - 90^\circ - P_{co} \quad (1)$$

(ii) Place the double zero at the LC network resonant frequency, f_o , to avoid oscillatory.

(iii) One pole, f_{p1} , is placed at f_{zRHP} to cancel the gain effect of RHP zero.

(iv) From (3), f_{p2} can be found as follows:

$$\tan^{-1}\left(\frac{f_{co}}{f_{p2}}\right) = \tan^{-1}\left(\frac{f_{co}}{f_{z1}}\right) + \tan^{-1}\left(\frac{f_{co}}{f_{z2}}\right) - \tan^{-1}\left(\frac{f_{co}}{f_{p1}}\right) - P_{boost} \equiv \Phi_{fp2} \quad (2)$$

$$f_{p2} = \frac{f_{co}}{\tan(\Phi_{fp2})}$$

(v) The gain of the integrator, ω_i , can be found as follows:

$$A_{co} = 10^{\frac{A_{co}dB}{20}} \quad G = \frac{1}{A_{co}} \quad \text{or} \quad G = 10^{\frac{-A_{co}dB}{20}} \quad (4)$$

$$\omega_i = (G)(2\pi f_{co}) \frac{\sqrt{\left(1 + \left(\frac{f_{co}}{f_{p1}}\right)^2\right)\left(1 + \left(\frac{f_{co}}{f_{p2}}\right)^2\right)}}{\sqrt{\left(1 + \left(\frac{f_{co}}{f_{z1}}\right)^2\right)\left(1 + \left(\frac{f_{co}}{f_{z2}}\right)^2\right)}}$$

$$f_{z1} = f_o, \quad f_{z2} = f_o, \quad f_{p1} = f_{zRHP}, \quad f_{p2} = \frac{f_{co}}{\tan(\Phi_{fp2})}$$

(vi) Let,

$$\begin{aligned} R_1 &= 4.7 \text{ k}\Omega \\ C_2 &= \frac{1}{\omega_i R_1 \frac{f_{p2}}{f_{z1}}} \\ C_1 &= C_2 \left(\frac{f_{p2}}{f_{z1}} - 1 \right) \\ R_2 &= \frac{1}{2\pi f_{z1} C_1} \\ R_3 &= \frac{R_1}{\left(\frac{f_{p1}}{f_{z2}} - 1 \right)} \\ C_3 &= \frac{1}{2\pi f_{p1} R_3} \\ R_{bias} &= \frac{V_{ref}}{V_o - V_{ref}} R_2 \end{aligned}$$